
Project Strawberry


Digital VLSI 2019

partner: William Meng

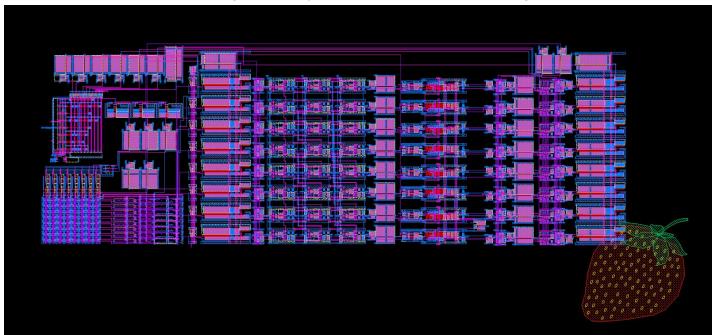A custom 8-bit microcontroller, designed and layed out in Cadence Virtuoso using 90nm CMOS.




The final product is shown above.

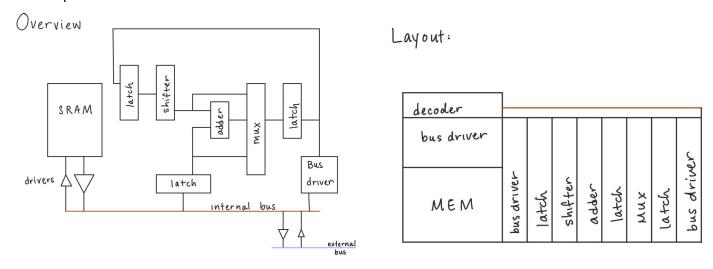


Below are closeups of the components in the 8-bit microcontroller.

8-bit 2's Complement Ripple Carry Adder:

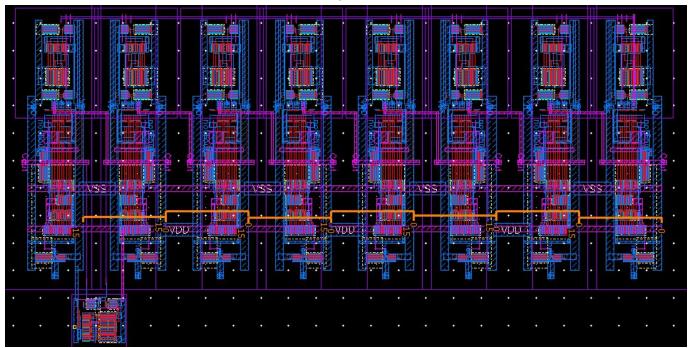- 8 one-bit 2's complement adders and an XOR gate for overflow detection




8 bit shifter created from muxes:

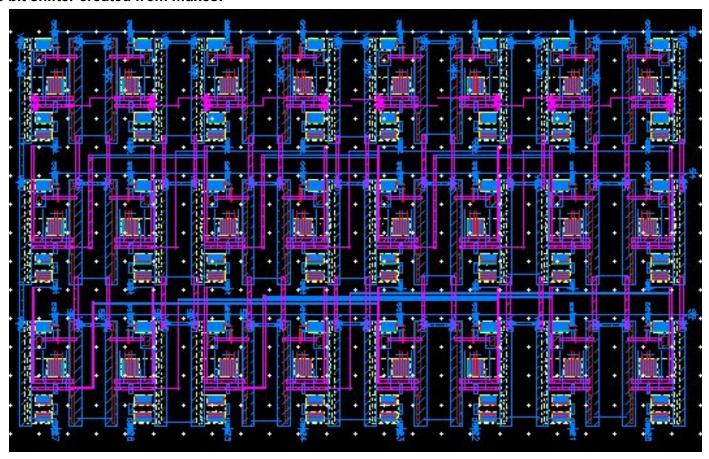


SRAM with single-ended read:

- 8 Wordlines
- decoder

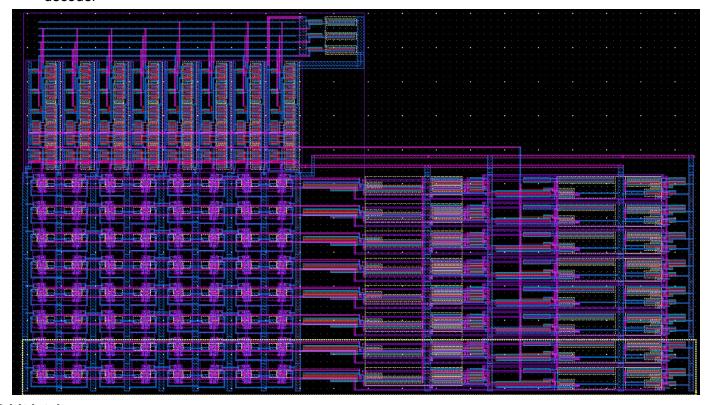


8-bit latch:

- A snippet of 4 latches

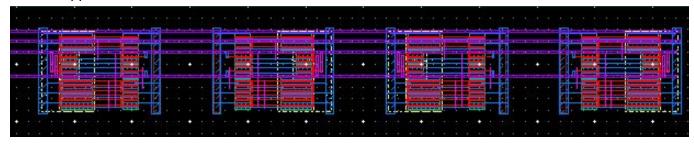


- Closeup of 1 one-bit latch

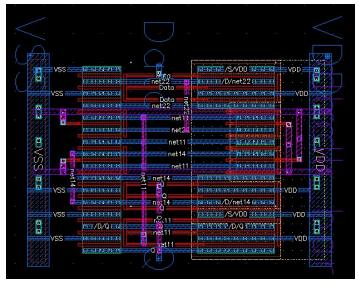


8-bit 3-1 MUX:


- Snippet of 5 3-1 one bit muxes

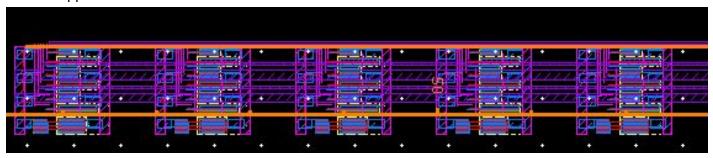



- Closeup of one 3-1 MUX

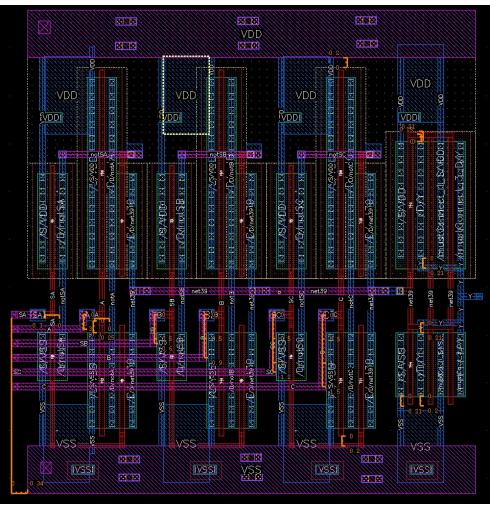

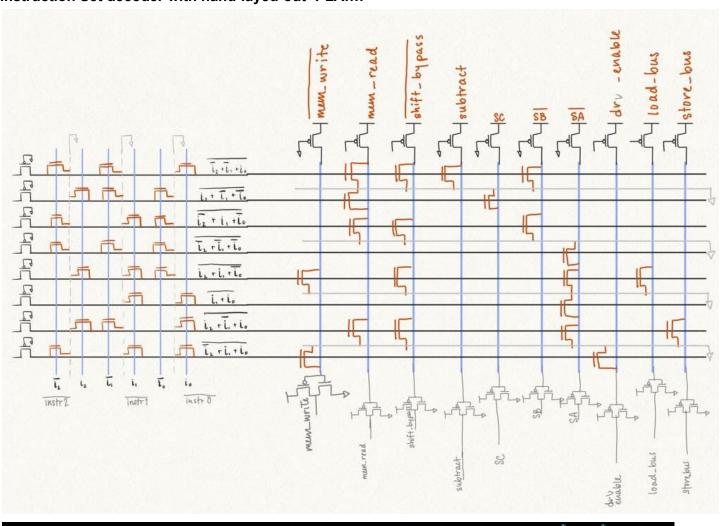Instruction Set decoder with hand-layed-out- PLA...:



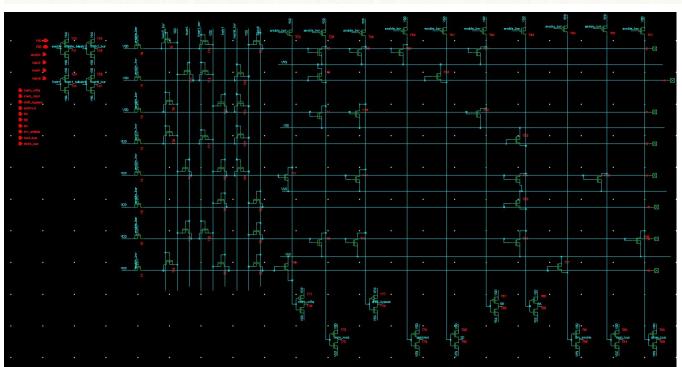

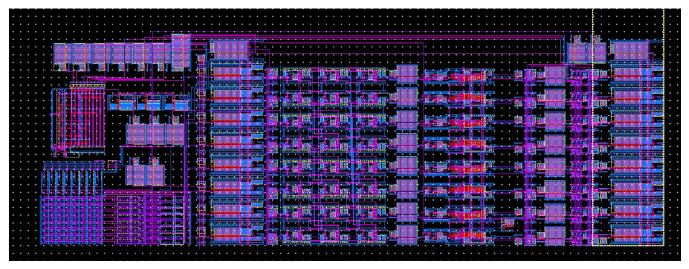

Voila!